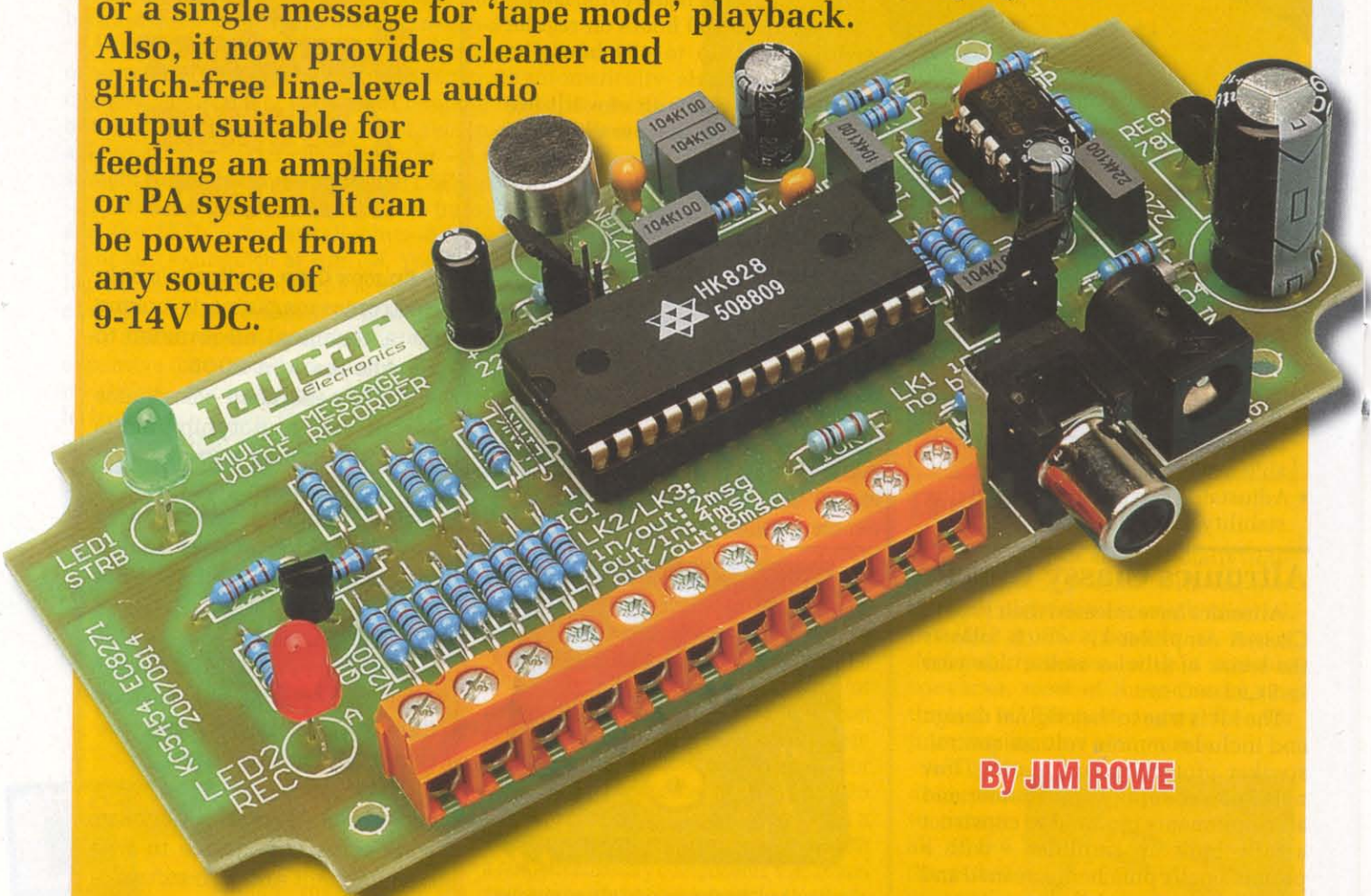


Here's an improved version of the very popular voice recorder design we published in May 2005. It can now be set up easily to record two, four or eight different messages for random-access playback or a single message for 'tape mode' playback.

Also, it now provides cleaner and glitch-free line-level audio output suitable for feeding an amplifier or PA system. It can be powered from any source of 9-14V DC.



By JIM ROWE

AN ENHANCED 45-SECOND VOICE RECORDER MODULE

The solid state voice recorder module published in the May 2005 issue of SILICON CHIP proved to be very popular. It has been used in all sorts of applications where messages or sounds needed to be recorded and played back reliably under either manual or micro control.

But it had limitations – one of which was that it could only be used to record and play back one long message or a number of short messages in sequential ‘tape recorder’ fashion.

This was despite the fact that the recorder chip we used was capable of recording and playing back up to eight messages in ‘random access’ mode. The module needed a fair bit of ‘hacking’ to make the chip work in this mode.

Another limitation was that the playback sound quality of the module was fairly noisy and each message played back was accompanied by an irritating ‘click’ at the start and finish. With the benefit of hindsight this was due to the way we had chosen to couple the output audio from only one side of the recorder chip’s push-pull output.

Hindsight also revealed a third limitation: the 2005 module had been designed to operate from a 6V battery, whereas many people wanted to use it from a nominal 12V DC source.

It was with these limitations in mind that we decided to develop the new and improved sound recorder module described here.

It’s based on the same HK828 chip used in the 2005 module but with the

rest of the circuit designed to allow more flexibility in terms of message storage and to provide much cleaner and click-free playback audio. Finally, the new circuit can run from any source of DC between 9V and 14V.

The HK828 chip has the ability to store single or multiple messages with a total length of between 40 and 60 seconds, depending on the sampling rate and the voice quality you want.

In this new recorder module the chip is again teamed up with a low-cost electret microphone to allow easy message recording, plus an LM358 dual op amp IC which allows the recorded messages to be played back as a line level audio signal available for feeding an external amplifier and speaker.

A suitable small amplifier for use with the module would be ‘The Champ’, as described in the February 1994 issue of SILICON CHIP. This is available at low cost (\$5.95) from Jaycar Electronics as KC-5152.

We’ve given the new module a set of ‘jumper links’ so it can be easily configured to record and play back messages in any of four modes: either two, four or eight messages in random access mode or one or more messages in sequential access ‘tape mode’. Another link allows the HK-828 chip’s message start ‘beeps’ to be enabled or disabled, as you wish.

All message selection, record and play functions are controlled externally, by connections to a row of screw terminals along the side of the module. All functions are enabled by switches

or logic signals. This makes it easy to record or play back messages using a set of pushbuttons and a switch or under the control of a PC, microcontroller or security system if you prefer.

By the way, since the HK828 voice recorder chip is only available from Jaycar Electronics in Australia and New Zealand, kits for the new recorder module will only be available from Jaycar and its dealers.


How it works

Because HK828 chip forms the functional heart of the recorder module, you need to have at least a rough idea of what goes on inside this chip in order to understand how the recorder works. Fig.1 shows the chip’s basic architecture.

First, the chip includes a high-gain microphone preamp so that it can be driven directly by a low cost electret microphone insert. An automatic gain control (AGC) circuit follows the preamp, to ensure that good quality recordings can be made without any need for manual gain adjustment, despite input signal level variations.

The output of the AGC circuit is not connected directly to the chip’s recording circuitry but is brought out to the ‘Aout’ pin instead. This is linked to the ‘Ain’ pin by the user, to record messages from the microphone. This arrangement allows the chip to be used to record from line level signals in other applications.

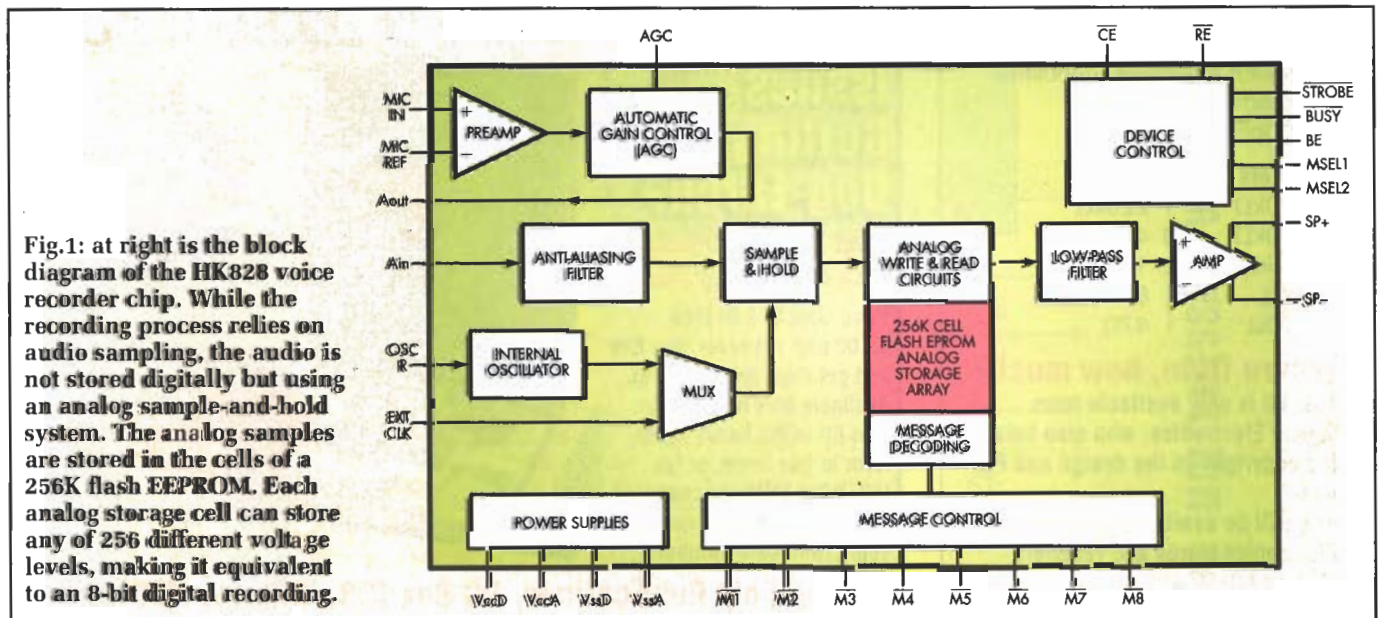Since the main part of the HK828 records by a process of sampling the audio signals fed into it via the Ain



Parts List – Enhanced Voice Recorder

- 1 PC board, code EC8271, 119 x 57mm
- 1 electret microphone insert (AM-4011)
- 3 3-way terminal blocks, PC board mtg
- 1 2-way terminal block, PC board mtg
- 3 2-pin sections of SIL header strip
- 3 jumper shunts
- 1 28-pin DIL IC socket, 15.24mm spacing
- 1 8-pin DIL IC socket, 7.62mm spacing
- 1 2.5mm concentric DC power plug, PC board mtg (CON1)
- 1 RCA audio socket, PC board mtg (CON2)

Semiconductors

- 1 HK828 voice recorder IC (IC1)
- 1 LM358 dual op amp (IC2)
- 1 78L05 +5V regulator (REG1)
- 1 PN200 PNP transistor (Q1)
- 1 5mm green LED (LED1)
- 1 5mm red LED (LED2)
- 1 1N4004 1A diode (D1)

Capacitors

- 1 2200 μ F 16V RB electrolytic
- 1 220 μ F 16V RB electrolytic
- 1 22 μ F 16V RB electrolytic
- 1 10 μ F 16V RB electrolytic
- 1 4.7 μ F 25V tag tantalum
- 1 220nF 100V MKT metallised polyester
- 5 100nF 100V MKT metallised polyester
- 1 100nF multilayer monolithic ceramic
- 1 150pF disc ceramic

Resistors (0.25W 1%)

- | | |
|-----------------|-----------------|
| 1 470k Ω | 1 220k Ω |
| 2 100k Ω | 8 47k Ω |
| 9 22k Ω | 2 10k Ω |
| 2 1k Ω | 2 680 Ω |
| 1 100 Ω | 1 47 Ω |

Where from, how much?

This kit is only available from Jaycar Electronics, who also hold the copyright on the design and PC board.

Kits will be available from Jaycar Electronics stores and resellers (Cat no KC-5454).

pin, it needs to pass these signals through a low-pass filter before the sampling. This is done to prevent distortion caused by sampling aliases, hence the "anti aliasing" filter between the "Ain" input and the sample and hold circuit block.

Now although the audio is sampled inside the HK828, this is done using an analog sample-and-hold system rather than the more common digital sampling system. It stores the samples in an array of 262,144 (256K) Flash EEPROM analog storage cells, each of which can store any of 256 different voltage levels. This gives the equivalent of 8-bit digital recording.

The capacity of the storage array means that the HK828 can store a total of 256K samples. How long a recorded message this gives depends on the sampling rate that's used.

For example, if the sample rate is 8000 samples per second, 256K samples will correspond to a total message length of just over 32 seconds (262,144/8000). However if you sample at 4200 samples/second, the 256K samples will give a total message length of just over 62 seconds (262,144/4200).

The recording bandwidth or 'fidelity' is directly proportional to the sampling rate. So if you sample at 4200 samples/second, the recording bandwidth will be just over 2kHz, whereas sampling at 8000 samples/second gives a bandwidth of just on 4kHz.

Choosing the sampling rate is there-

fore of a compromise: the lower the sampling rate the longer the recording time but the lower the audio bandwidth. Conversely, the higher the sampling rate the higher the bandwidth but the shorter the recording time.

The HK828 chip has an internal sampling rate clock oscillator, as well as an input for an optional external clock. Either clock signal can be fed to the sample and hold circuit via the multiplexer (MUX), to control the sampling.

The frequency of the internal oscillator is set by varying the value of an external resistor connected between the 'OscR' pin and ground. Our circuit uses a 47k Ω resistor, which sets the sampling rate to about 5800 samples/second. This gives a message recording time of about 45 seconds and a bandwidth of about 2.9kHz, for reasonable voice-quality recording.

As shown in Fig.1, the recording and playback of samples in the storage array is controlled by analog write and read circuits, along with the message control and message decoding circuits. When a message is being played back the signals pass through another low-pass filter to remove sampling noise, and are then fed to the inbuilt output amplifier.

The rest of the circuitry inside the HK828 chip is used for overall device control, mode switching and so on.

Circuit details

Fig.2 shows the complete circuit

Silicon Chip Binders

Issues Getting Dog-Eared?


Keep Your Copies Safe With These Handy Binders

Price: Just \$13.95 plus \$7.00 p&p per order (buy five and get them postage free). Available only in Australia. Just fill in the handy order form in this issue; or fax (02) 9939 2648; or phone (02) 9939 3295 and quote your credit card number.



REAL VALUE AT \$13.95 PLUS P&P

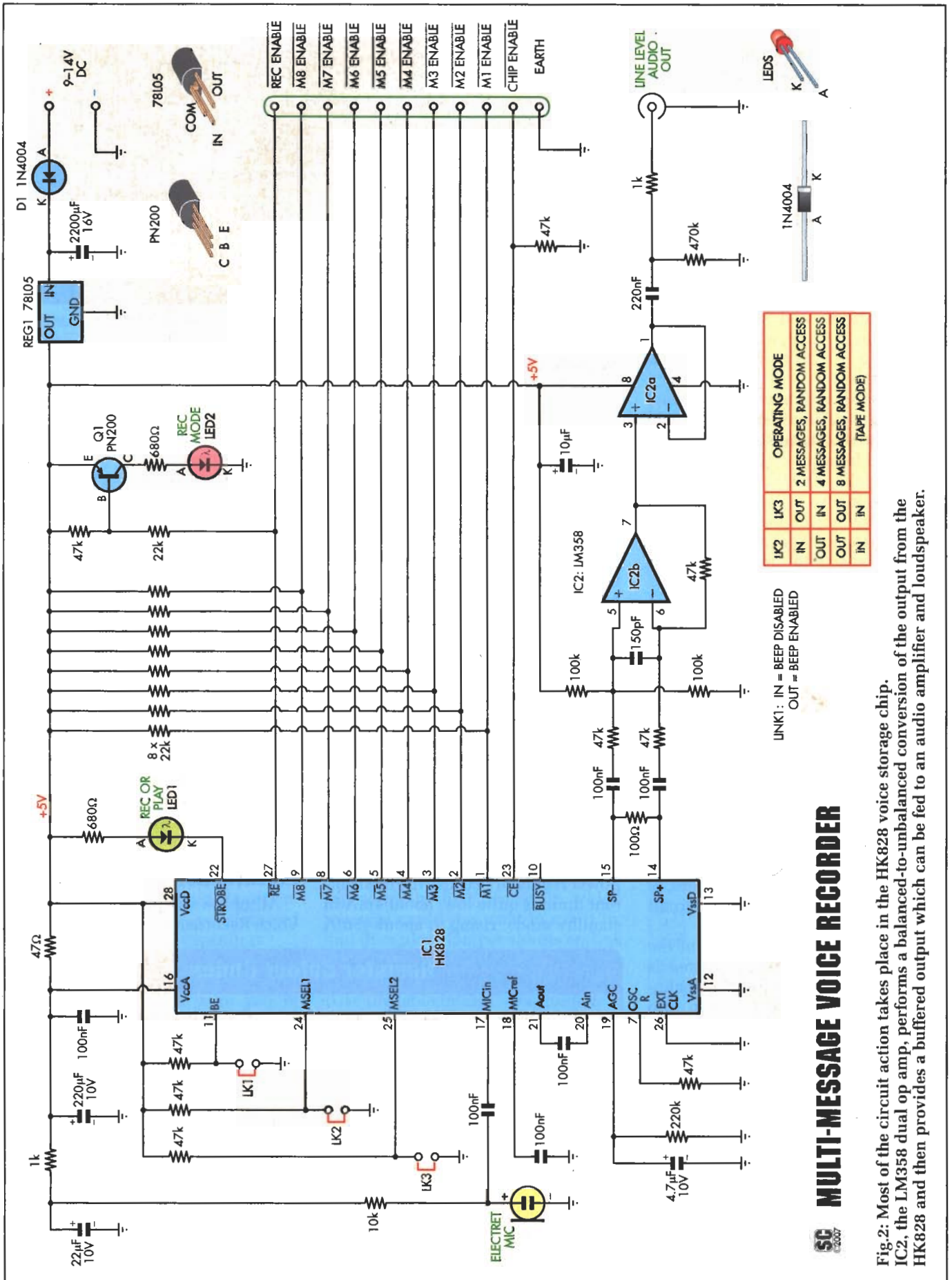Silicon Chip Publications, PO Box 139, Collaroy NSW 2097.




IK2	IK3	OPERATING MODE
IN	OUT	2 MESSAGES, RANDOM ACCESS
OUT	IN	4 MESSAGES, RANDOM ACCESS
OUT	OUT	8 MESSAGES, RANDOM ACCESS (TAPE MODE)
IN	IN	

LINK1: IN = BEEP DISABLED
OUT = BEEP ENABLED

SC MULTI-MESSAGE VOICE RECORDER

Fig. 2: Most of the circuit action takes place in the HK828 voice storage chip. IC2, the LM358 dual op amp, performs a balanced-to-unbalanced conversion of the output from the HK828 and then provides a buffered output which can be fed to an audio amplifier and loudspeaker.

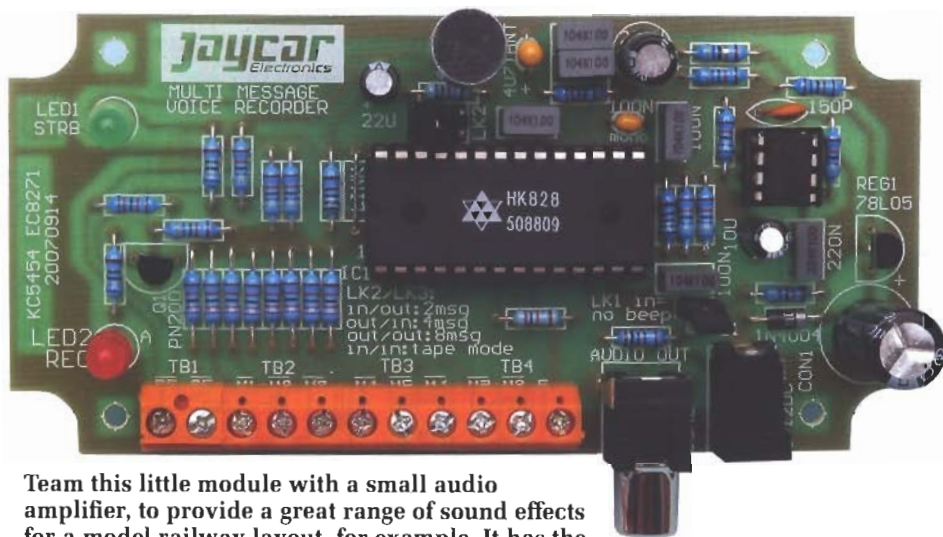

Team this little module with a small audio amplifier, to provide a great range of sound effects for a model railway layout, for example. It has the ability to store up to eight different "sound grabs" which could be switched to different parts of the layout as trains pass through stations.

PC board. This is coded EC8271, and measures 107 x 57mm. It can be mounted inside a standard UB3 size jiffy box. As all of the terminals and connectors are along one side the board, they will all be accessible via a slot or series of holes along that side of the box. Only three holes will be needed in the box lid: two 5mm holes for LED1 and LED2, and a larger hole to allow sound to reach the electret mic insert.

The location and orientation of all components on the board can be seen in the overlay diagram of Fig.3, and also in the matching photo of the module.

Start board assembly by fitting the four screw terminal blocks, then the DC input and audio output sockets. Follow these with the two IC sockets, the three 2-pin headers for LK1-LK3 and the short wire link which fits just near the end of the 28-pin IC socket. After this you can fit the resistors and smaller non-polarised capacitors.

Next come the 4.7µF tantalum and the electrolytic capacitors, which are all polarised, so make sure you fit them with their orientation as shown in the diagram.

Now you'll be ready to fit the semiconductor parts. These are again all polarised, so make sure you follow

the diagram carefully as a guide to their orientation. Fit diode D1 first, then transistor Q1 and the two LEDs, followed by regulator REG1.

Then fit the electret mic insert. This has only two wire leads, but it is polarised, so make sure you check the back of the insert to make sure which lead connects to the metal body of the insert. This is the negative lead, which must be connected to the earthy outer pad under the board. The other lead is the positive lead.

Finally, plug the LM358 op amp IC2 into its 8-pin socket and the larger HK828 chip IC1 into its 28-pin socket. Make sure they're both orientated as shown in Fig.3. Your Multi-Message Voice Recorder should now be complete and ready to go.

Trying it out

To check that your recorder is working correctly, first decide on which message mode you want to use it in, and then place jumper shunts on link headers LK1, LK2 and LK3 to set the module for that mode of operation. (Use the table in Fig.2 as a guide.)

Then connect a small toggle switch and one pushbutton switch for each message you want to select to the appropriate screw terminals of the module, as shown in Fig.4. For the present switch the toggle switch off, which corresponds to message playback mode.

The audio output of the module can now be connected to the line input of any suitable audio amplifier. Then you can connect its DC power input to a source of 9-14V DC.

JOIN THE TECHNOLOGY AGE NOW with PICAXE



Developed as a teaching tool, the PICAXE is a low-cost "brain" for almost any project

Easy to use and understand, professionals & hobbyists can be productive within minutes.

Free software development system and low-cost in-circuit programming.

Variety of hardware, project boards and kits to suit your application.

Digital, analog, RS232, 1-Wire™, SPI and I²C. PC connectivity.

Applications include:

Datalogging

Robotics

Measurement & instruments

Motor & lighting control

Farming & agriculture

Internet server

Wireless links

Colour sensing

Fun games



Distributed in Australia by

Microzed Computers Pty Limited

Phone 1300 735 420

Fax 1300 735 421

www.microzed.com.au

Capacitor Codes

Value	µF Code	IEC Code	EIA Code
220nF	0.22µF	220n	224
100nF	0.1µF	100n	104
150pF	n/a	150p	151

At this stage neither of the LEDs should light but you may hear a small turn-on 'plop' from the speaker connected to the external amplifier. If you wish you can use a digital multimeter to confirm that the supply voltage at pin 8 of IC2 is very close to +5V, relative to the module's earth terminal.

Now switch the external toggle switch on, pulling the RecEnable-bar line down to earth potential. This should switch the module into Record mode, so LED2 should begin glowing. (If it doesn't begin glowing, you either have the DC power polarity reversed, or LED2 fitted to the board the wrong way around.)

Next, press one of the message select pushbuttons – say MSG1 in Fig.4. Holding it down, begin talking into the electret mic to record your test message.

As you speak, you'll notice that the green Strobe LED (LED1) is flashing. Keep talking until you reach the end of your message or until LED1 stops flashing (which indicates that recording has stopped automatically, because you have reached the end of that segment of the HK828's memory). Then release the pushbutton.

To replay the recorded message, turn the toggle switch off to swing the module into Play mode and briefly press the message pushbutton again, but this time only briefly because in Play mode, the message buttons only trigger the replay operation.

Your recorded message should then be replayed through the external amplifier and speaker. If it does, your Multi-Message Voice Recorder is working correctly and should now be ready for use.


Changing message length

As mentioned earlier, the total message length stored in the HK828 chip's memory is determined by the sampling rate which is set by the resistor connected from pin 7 of the chip (OscR) to ground.

The 47k Ω value shown for this resistor in the circuit and overlay diagram gives a sampling rate of 5800 samples/second, resulting in a total message length of 45 seconds and an audio bandwidth of about 2.9kHz.

We picked this as a reasonable compromise between message length and recording quality but you can experiment with the value of this resistor to try longer/shorter recording times and

Fig.4: Staying with the model rail theme, you could use reed relays or other switches to play back the sound grabs when the train triggers them or they are switched by the operator. If the sound grabs played in different locations you will need additional speakers and relays to switch them to the amplifier.

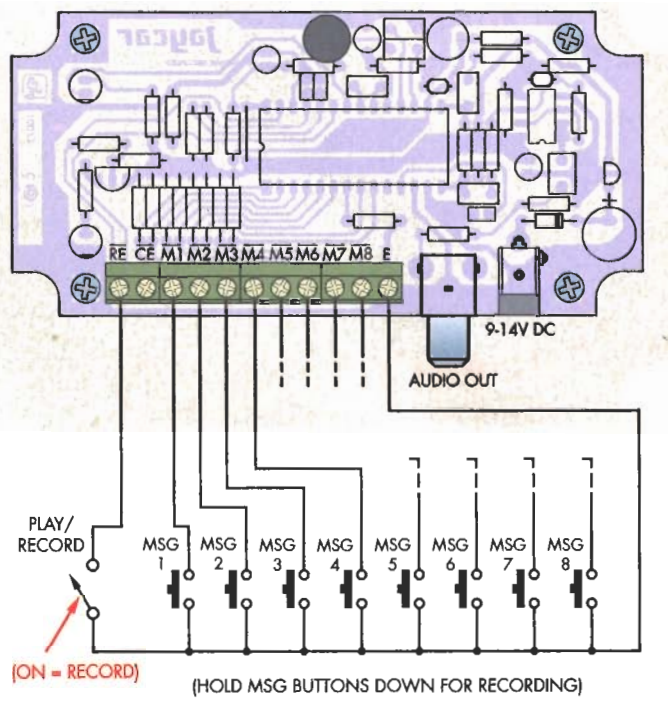

narrower/wider audio bandwidth.

For example, if you change the resistor value to 82k Ω , this will lower the sampling rate to about 4200 samples/second and give a total recording time of just on 60 seconds. However the audio bandwidth will also drop to around 2kHz, so the played-back message(s) will sound rather 'muffled' – a bit like talking through a wet sock!

On the other hand, if you lower the resistor value to 24k Ω , this will increase the sampling rate to about 8000 samples/second and drop the recording time to just on 32 seconds. But the recording quality will improve, as the audio bandwidth will increase to about 4kHz.

So experiment by all means, and settle on the resistor value you decide gives the best combination of total message length and acceptable audio quality for your application.

Changing message mode

As noted earlier, header links LK2 and LK3 on the board can be used to change the module's message access mode.

For example with a jumper shunt fitted to LK2 but removed from LK3, the module will be able to record and play two messages (each using half the HK828's memory space). You'll only need two external pushbuttons to select one of these messages: MSG1

and MSG2, along with the Record/Play toggle switch.

If you want to record and play four messages, remove the jumper shunt from LK2 and place one on LK3 instead. You'll now need four external pushbuttons as well as the Record/Play toggle switch: MSG1, MSG2, MSG3 and MSG4. Note that in this case each message will be able to use one quarter of the HK828's memory.

Leave the jumper shunts off both LK2 and LK3 if you want to record and play any of eight short messages (each using one eighth of the HK828's memory). You'll now need all eight external pushbuttons MSG1 - MSG8, along with the Record/Play toggle switch.

The last option is to fit jumper shunts to both LK2 and LK3, which sets the module for "tape mode" operation.

In this mode you normally only need one external pushbutton (MSG1), because the HK828 records and plays back either one message or a sequence of messages, using all of its memory space.

That's it then – an easy-to-build solid state Multi-Message Voice Recorder module that can be used for all kinds of applications, especially those involving sending pre-recorded messages over an amplifier or PA system under the control of a PC or microcontroller.

